

Circuit Demonstration Page

Student names:

Kyle MonkJane Ross

Instructor Initials

Pushbutton "Or Gate"

BD

Transistor Not gate

BD

Transistor Nor gate

BD


Transistor unknown gate

BD

Diagrams

On each of the circuits below, draw the current paths and note whether each switch, transistor, and LED is ON or OFF.

Inverter:

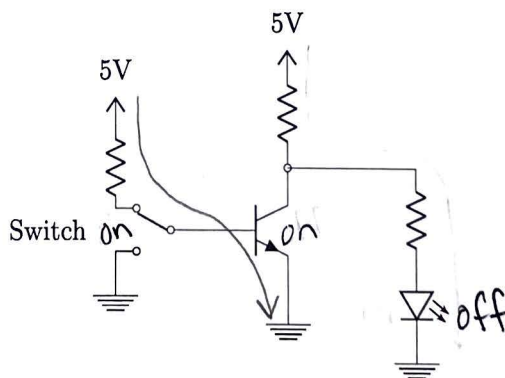

0	1
1	0

