

ELC 2137 Lab 2: Transistor Logic Gates

Kyle Monk and Jane Ross

January 29, 2020

Summary

In this lab, circuits were constructed to act as logic gates. To do this, several resistors and transistors were connected to switches and lights. Based on if the light was on or off, it was possible to determine the flow of current through the transistors and if the transistors were acting as "on" or "off". Transistors are "voltage-controlled switches", so they were on or off depending on whether or not there was current flowing through them. Diagrams were given as a guide on how to construct the three circuits in the lab. There were varying amounts of transistors and switches used in each circuit to create an inverter gate, a nor gate, and an and gate.

Questions

1. Logic/truth table for Final gate

Switch 1	Switch 2	Light
0	0	0
0	1	0
1	0	0
1	1	1

2. This circuit implements an And gate because the light does not come on unless both switches are on.

Circuit Demonstration Page

Student names: Kyle Monk Jane Ross

Instructor Initials

Pushbutton "Or Gate"

BD

Transistor Not gate

BD

Transistor Nor gate

BD


Transistor unknown gate

BD

Diagrams


On each of the circuits below, draw the current paths and note whether each switch, transistor, and LED is ON or OFF.

Inverter:

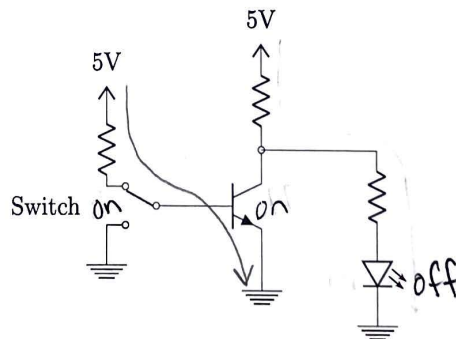

0 1
1 0

NOR:

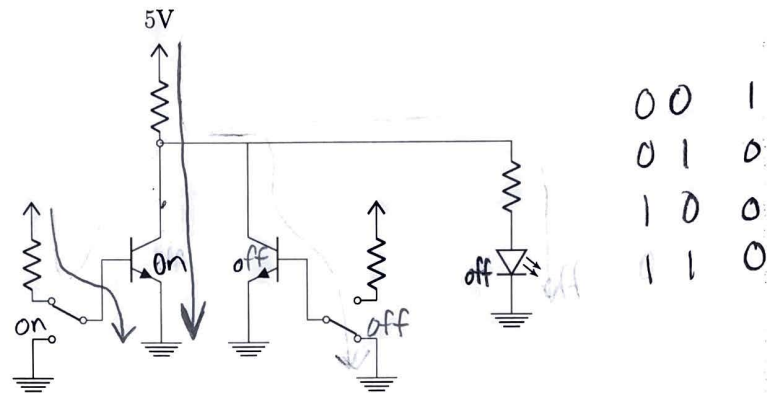

Final gate:

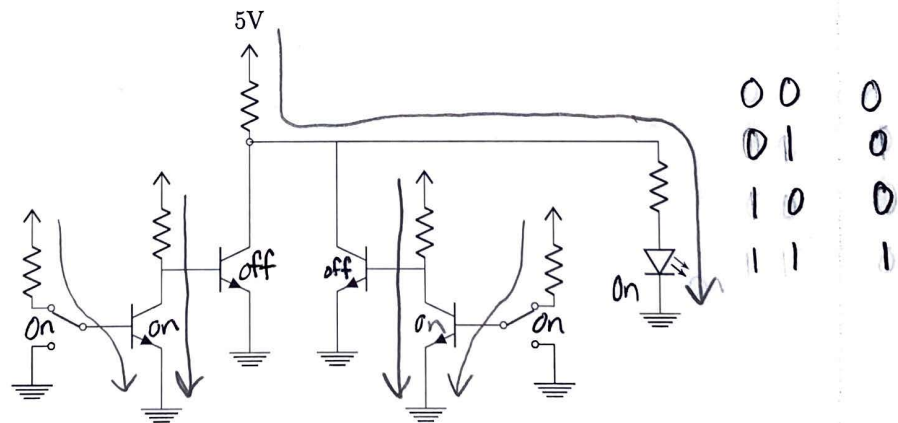


Figure 1: Results: Circuit Demonstration Pages